

1	A	B	C	D	A'	B'	C'	D'	$A \cdot B \cdot C \cdot D'$	$(B \cdot C \cdot D)'$	$A \cdot (B \cdot C \cdot D)'$	$(A+B+C+D)$	$A \cdot B \cdot C \cdot D' + A \cdot (B \cdot C \cdot D)' + (A+B+C+D)'$
0	0	0	0	1	1	1	1	0	0	1	0	1	1
0	0	0	1	1	1	1	0	0	0	1	0	0	0
0	0	1	0	1	1	0	1	0	0	1	0	0	0
0	0	1	1	1	1	0	0	0	0	1	0	0	0
0	1	0	0	1	0	1	1	0	0	1	0	0	0
0	1	0	1	1	0	1	0	0	0	1	0	0	0
0	1	1	0	1	0	0	1	0	0	1	0	0	0
0	1	1	1	0	0	0	1	0	0	1	0	0	0
1	0	0	0	1	1	1	0	0	0	0	0	0	0
1	0	0	1	1	1	1	0	0	0	0	0	0	0
1	0	1	0	1	0	0	1	0	0	0	0	0	0
1	0	1	1	0	0	0	0	0	0	0	0	0	0
1	1	0	0	0	1	1	1	0	0	0	0	0	0
1	1	0	0	1	1	1	0	0	0	0	0	0	0
1	1	0	1	0	1	0	1	0	0	0	0	0	0
1	1	0	1	1	0	0	0	0	0	0	0	0	0
1	1	1	0	0	0	0	1	0	0	0	0	0	0
1	1	1	0	1	0	0	0	0	0	0	0	0	0
1	1	1	1	0	0	0	0	0	0	0	0	0	0

		AB			
CD		00	01	11	10
	00	1	0	1	1
	01	0	0	1	1
	11	0	0	0	1
	10	0	0	1	1

$Y = B'C'D' + AC' + AB' + ACD'$

A	B	C	D	Y
0	0	0	0	1
0	x	x	x	0
1	x	x	x	1
1	1	1	1	0

2	A	B	C	A'	B'	C'		$A' \cdot B \cdot C$	$B \cdot C'$	$(B \cdot C)'$	$B \cdot C$	$A' \cdot B \cdot C + (B \cdot C)' + B \cdot C$
0	0	0	1	1	1	1		0	0	1	0	1
0	0	1	1	1	0			0	0	1	0	1
0	1	0	1	1	0			0	1	0	0	0
0	1	1	0	0				1	0	1	1	1
1	0	0	0	1	1			0	0	1	0	1
1	0	1	0	1	0			0	0	1	0	1
1	1	0	0	1				0	1	0	0	0
1	1	1	0	0				0	1	0	0	0
1	1	1	1	0	0			0	0	1	1	1

		AB			
C		00	01	11	10
	0	1	0	0	1
	1	1	1	1	1

$Y = C + B'$

A	B	C	Y
0	0	x	1
x	1	0	0
0	1	1	1
1	0	x	1
1	1	1	1

3	A	B	C	D	A'	B'	C'	D'	$A+B+C$	$(A+B+C)'$	$(A+B+C)' \cdot D$	$A \cdot D$	$Y = (A+B+C)' \cdot D + A \cdot D + B$
0	0	0	0	1	1	1	1	0	0	1	0	0	0
0	0	0	1	1	1	1	0	0	0	1	1	0	1
0	0	1	0	1	1	0	1	0	1	0	0	0	0
0	0	1	1	1	0	0			1	0	0	0	0
0	1	0	0	1	0	1	1	0	1	0	0	0	1
0	1	0	1	1	0	1	0	0	1	0	0	0	1
0	1	1	0	1	0	0	1	1	1	0	0	0	1
0	1	1	1	0	0	0	0	0	1	0	0	0	1
1	0	0	0	1	1	1	1	0	1	0	0	0	0
1	0	0	1	0	1	1	0	1	1	0	0	1	1
1	0	1	0	0	1	0	1	1	1	0	0	0	0
1	0	1	1	0	1	0	0	0	1	0	0	1	1
1	1	0	0	0	0	1	1	0	1	0	0	0	1
1	1	1	0	0	0	0	1	1	1	0	0	0	1
1	1	1	1	0	0	0	0	0	1	0	0	1	1

		AB			
CD		00	01	11	10
	00	0	1	1	0
	01	1	1	1	1
	11	0	1	1	1
	10	0	1	1	0

$Y = B + C'D + AB'D$

A	B	C	D	Y
0	0	x	x	0
0	x	0	x	1
0	1	1	x	1
1	0	x	0	0
1	x	x	x	1

	A	B	C	A'	B'	C'		$B \cdot C$	$A' \cdot B' \cdot C'$	$B \cdot C'$		$B \cdot C + A' \cdot B' \cdot C' + B \cdot C'$
0	0	0	1	1	1	1		0	1	0		1
0	0	1	1	1	0			0	0	0		0
0	1	0	1	0	1			0	0	1		1
0	1	1	1	0	0			1	0	0		1
1	0	0	0	1	1			0	0	0		0
1	0	1	0	1	0			0	0	0		0
1	1	0	0	0	1			0	0	1		1
1	1	1	0	0	0			1	0	0		1

		AB			
C		00	01	11	10
	0	1	1	1	0
	1	0	1	1	0

$Y = B + A'C'$

A	B	C	Y
0	x	x	1
0	0	1	0
1	0	x	0
1	1	x	1

```

//Diego Alejandro Mendez
//Carnet 19673
//Ejercicio 04
module E1_1GL(input wire A, B, C, output wire Y1);
//ejercicio 1.1 con GateLevel Modeling

    wire outAN, outBN, outCN, out01, out02, out03, out04;

//not's
    not U1 (outAN,A);
    not U2 (outBN,B);
    not U3 (outCN,C);

//compuertas

    and U4 (out01, outAN, outCN);
    and U5 (out02, A, C);
    and U6 (out03, A, outBN);
    or U7 (Y1, out01, out02, out03);
endmodule

module E1_2GL(input wire A, B, C, output wire Y2);
//ejercicio 1.2 con GateLevel Modeling

    wire outAN, outBN, outCN, out01, out02, out03, out04;

//not's
    not U2 (Y2,B);

endmodule

module E1_3OP(input wire A, B, C, D, output wire Y3);
//ejercicio 1.3 con operadores
    assign Y3 = (~A & ~B & ~C & ~D) | (~A & ~B & C & D) | (~A & B & ~C & D) | (~A & B & C & ~D) | (A & B & ~C & ~D) | (A & B & C & D) | (A & ~B & ~C & D) | (A & ~B & C & ~D);

endmodule

module E1_4GL (input wire A, B, C, D, output wire Y4);
//Ejercicio 1.4 con GateLevel Modeling

    wire outAN, outBN, outCN, outDN, out01, out02, out03, out04;
//not's
    not U1 (outAN,A);
    not U2 (outBN,B);
    not U3 (outCN,C);

```

```

    not U4 (outDN,D);

//compuertas

    and U5(out01, A, B);
    and U6(out02, A, outCN, outDN);
    and U7(out03, A, B, C);
    or U8(Y4, out01, out02, out03);
endmodule //E1_4

module E2_1OP (input wire A, B, C, D, output wire Y5);
//Ejercicio 2.1 con operadores
    assign Y5 = (~B & ~C & ~D) | (A & ~C) | (A & ~B) | (A & C & ~D);

endmodule // E2_1OP

module E2_2GL (input A, B, C, output wire Y6);
//Ejercicio 2.2 con GateLevel Modeling

//Not's
    not U1 (outAN,A);
    not U2 (outBN,B);
    not U3 (outCN,C);

//compuertas
    or U5 (Y6, C, outBN);

endmodule // E2_2GL

module E2_3OP (input A, B, C, D, output wire Y7);

    assign Y7= (B) | (~C & D) | (A & ~B & D);

endmodule // E2_3OP

module E2_4OP (input A, B, C, output wire Y8);

    assign Y8 = (B) | (~A & ~C);

endmodule // E2_4OP

```

```

//Diego Alejandro Mendez
//Carnet 19673
//Ejercicio 05
module testbench();
// registrar entradas
    reg inA1, inB1, inC1;
    reg inA2, inB2, inC2;
    reg inA3, inB3, inC3, inD3;
    reg inA4, inB4, inC4, inD4;
    reg inA5, inB5, inC5, inD5;
    reg inA6, inB6, inC6;
    reg inA7, inB7, inC7, inD7;
    reg inA8, inB8, inC8;

    wire Y1, Y2, Y3, Y4, Y5, Y6, Y7, Y8;

    E1_1GL E1(inA1, inB1, inC1, Y1);
    E1_2GL E2(inA2, inB2, inC2, Y2);
    E1_3OP E3(inA3, inB3, inC3, inD3, Y3);
    E1_4GL E4(inA4, inB4, inC4, inD4, Y4);
    E2_1OP E5(inA5, inB5, inC5, inD5, Y5);
    E2_2GL E6(inA6, inB6, inC6, Y6);
    E2_3OP E7(inA7, inB7, inC7, inD7, Y7);
    E2_4OP E8(inA8, inB8, inC8, Y8);

    initial begin
        $display(" ");           //iniciamos el módulo Ej1.1
        $display("EJERCICIO 1.1");
        $display("A B C | Y");
        $display("-----");
        $monitor("%b %b %b %b", inA1, inB1, inC1, Y1);
        inA1=0; inB1=0; inC1=0;
        #1 inA1=0; inB1=0; inC1=1;
        #1 inA1=0; inB1=1; inC1=0;
        #1 inA1=0; inB1=1; inC1=1;
        #1 inA1=1; inB1=0; inC1=0;
        #1 inA1=1; inB1=0; inC1=1;
        #1 inA1=1; inB1=1; inC1=0;
        #1 inA1=1; inB1=1; inC1=1;
    end

    initial begin                //iniciamos el módulo Ej1.2
        #9
        $display("");
    end

```

```

initial begin                                     //iniciamos el módulo Ej1.2
    #9
    $display("");
    $display("EJERCICIO 1.2");
    $display("A B C | Y");
    $display("-----");
    $monitor("%b %b %b %b",inA2,inB2,inC2,Y2);
        inA2=0; inB2=0; inC2=0;
    #1 inA2=0; inB2=0; inC2=1;
    #1 inA2=0; inB2=1; inC2=0;
    #1 inA2=0; inB2=1; inC2=1;
    #1 inA2=1; inB2=0; inC2=0;
    #1 inA2=1; inB2=0; inC2=1;
    #1 inA2=1; inB2=1; inC2=0;
    #1 inA2=1; inB2=1; inC2=1;
end

initial begin
    #18
    $display(" ");                                     //iniciamos el módulo Ej1.3
    $display("EJERCICIO 1.3");
    $display("A B C D | Y");
    $display("-----");
    $monitor("%b %b %b %b %b",inA3,inB3,inC3,inD3,Y3);
        inA3=0; inB3=0; inC3=0; inD3=0;
    #1 inA3=0; inB3=0; inC3=0; inD3=1;
    #1 inA3=0; inB3=0; inC3=1; inD3=0;
    #1 inA3=0; inB3=0; inC3=1; inD3=1;
    #1 inA3=0; inB3=1; inC3=0; inD3=0;
    #1 inA3=0; inB3=1; inC3=0; inD3=1;
    #1 inA3=0; inB3=1; inC3=1; inD3=0;
    #1 inA3=0; inB3=1; inC3=1; inD3=1;
    #1 inA3=1; inB3=0; inC3=0; inD3=0;
    #1 inA3=1; inB3=0; inC3=0; inD3=1;
    #1 inA3=1; inB3=0; inC3=1; inD3=0;
    #1 inA3=1; inB3=0; inC3=1; inD3=1;
    #1 inA3=1; inB3=1; inC3=0; inD3=0;
    #1 inA3=1; inB3=1; inC3=0; inD3=1;
    #1 inA3=1; inB3=1; inC3=1; inD3=0;
    #1 inA3=1; inB3=1; inC3=1; inD3=1;
end

```

```

initial begin
    #35
    $display(" ");          //iniciamos el módulo Ej1.4
    $display("EJERCICIO 1.4");
    $display("A B C D | Y");
    $display("-----");
    $monitor("%b %b %b %b %b",inA4,inB4,inC4,inD4,Y4);
    inA4=0; inB4=0; inC4=0; inD4=0;
    #1 inA4=0; inB4=0; inC4=0; inD4=1;
    #1 inA4=0; inB4=0; inC4=1; inD4=0;
    #1 inA4=0; inB4=0; inC4=1; inD4=1;
    #1 inA4=0; inB4=1; inC4=0; inD4=0;
    #1 inA4=0; inB4=1; inC4=0; inD4=1;
    #1 inA4=0; inB4=1; inC4=1; inD4=0;
    #1 inA4=0; inB4=1; inC4=1; inD4=1;
    #1 inA4=1; inB4=0; inC4=0; inD4=0;
    #1 inA4=1; inB4=0; inC4=0; inD4=1;
    #1 inA4=1; inB4=0; inC4=1; inD4=0;
    #1 inA4=1; inB4=0; inC4=1; inD4=1;
    #1 inA4=1; inB4=1; inC4=0; inD4=0;
    #1 inA4=1; inB4=1; inC4=0; inD4=1;
    #1 inA4=1; inB4=1; inC4=1; inD4=0;
    #1 inA4=1; inB4=1; inC4=1; inD4=1;
end

initial begin
    #52
    $display(" ");          //iniciamos el módulo Ej2.1
    $display("EJERCICIO 2.1");
    $display("A B C D | Y");
    $display("-----");
    $monitor("%b %b %b %b %b",inA5,inB5,inC5,inD5,Y5);
    inA5=0; inB5=0; inC5=0; inD5=0;
    #1 inA5=0; inB5=0; inC5=0; inD5=1;
    #1 inA5=0; inB5=0; inC5=1; inD5=0;
    #1 inA5=0; inB5=0; inC5=1; inD5=1;
    #1 inA5=0; inB5=1; inC5=0; inD5=0;
    #1 inA5=0; inB5=1; inC5=0; inD5=1;
    #1 inA5=0; inB5=1; inC5=1; inD5=0;
    #1 inA5=0; inB5=1; inC5=1; inD5=1;
    #1 inA5=1; inB5=0; inC5=0; inD5=0;
    #1 inA5=1; inB5=0; inC5=0; inD5=1;
    #1 inA5=1; inB5=0; inC5=1; inD5=0;
    #1 inA5=1; inB5=0; inC5=1; inD5=1;
    #1 inA5=1; inB5=1; inC5=0; inD5=0;

```

```

#1 inA5=1; inB5=1; inC5=1; inD5=0;
#1 inA5=1; inB5=1; inC5=1; inD5=1;
end

initial begin
    #70
    $display(" ");           //iniciamos el módulo Ej2.2
    $display("EJERCICIO 2.2");
    $display("A B C | Y");
    $display("-----");
    $monitor("%b %b %b %b",inA6,inB6,inC6,Y6);
    inA6=0; inB6=0; inC6=0;
#1 inA6=0; inB6=0; inC6=1;
#1 inA6=0; inB6=1; inC6=0;
#1 inA6=0; inB6=1; inC6=1;
#1 inA6=1; inB6=0; inC6=0;
#1 inA6=1; inB6=0; inC6=1;
#1 inA6=1; inB6=1; inC6=0;
#1 inA6=1; inB6=1; inC6=1;
end

initial begin
    #87
    $display(" ");           //iniciamos el módulo Ej2.3
    $display("EJERCICIO 2.3");
    $display("A B C D | Y");
    $display("-----");
    $monitor("%b %b %b %b %b",inA7, inB7, inC7, inD7,Y7);
    inA7=0; inB7=0; inC7=0; inD7=0;
#1 inA7=0; inB7=0; inC7=0; inD7=1;
#1 inA7=0; inB7=0; inC7=1; inD7=0;
#1 inA7=0; inB7=0; inC7=1; inD7=1;
#1 inA7=0; inB7=1; inC7=0; inD7=0;
#1 inA7=0; inB7=1; inC7=0; inD7=1;
#1 inA7=0; inB7=1; inC7=1; inD7=0;
#1 inA7=0; inB7=1; inC7=1; inD7=1;
#1 inA7=1; inB7=0; inC7=0; inD7=0;
#1 inA7=1; inB7=0; inC7=0; inD7=1;
#1 inA7=1; inB7=0; inC7=1; inD7=0;
#1 inA7=1; inB7=0; inC7=1; inD7=1;
#1 inA7=1; inB7=1; inC7=0; inD7=0;
#1 inA7=1; inB7=1; inC7=0; inD7=1;
#1 inA7=1; inB7=1; inC7=1; inD7=0;
#1 inA7=1; inB7=1; inC7=1; inD7=1;
end

```

```

initial begin
    #104
        $display(" ");           //iniciamos el módulo Ej2.4
        $display("EJERCICIO 2.4");
        $display("A B C | Y");
        $display("-----");
        $monitor("%b %b %b  %b",inA8, inB8, inC8, Y8);
        inA8=0; inB8=0; inC8=0;
    #1 inA8=0; inB8=0; inC8=1;
    #1 inA8=0; inB8=1; inC8=0;
    #1 inA8=0; inB8=1; inC8=1;
    #1 inA8=1; inB8=0; inC8=0;
    #1 inA8=1; inB8=0; inC8=1;
    #1 inA8=1; inB8=1; inC8=0;
    #1 inA8=1; inB8=1; inC8=1;
end

initial
#125 $finish;


initial begin



    $dumpfile("ejercicios_tb.vcd");
    $dumpvars(0,testbench);
end


endmodule

```

<p>EJERCICIO 1.1</p> <p>A B C Y</p> <p>-----</p> <p>VCD info: dumpfile</p> <p>0 0 0 1</p> <p>0 0 1 0</p> <p>0 1 0 1</p> <p>0 1 1 0</p> <p>1 0 0 1</p> <p>1 0 1 1</p> <p>1 1 0 0</p> <p>1 1 1 1</p>	<p>EJERCICIO 1.3</p> <p>A B C D Y</p> <p>-----</p> <p>0 0 0 0 1</p> <p>0 0 0 1 0</p> <p>0 0 1 0 0</p> <p>0 0 1 1 1</p> <p>0 1 0 0 0</p> <p>0 1 0 1 1</p> <p>0 1 1 0 1</p> <p>0 1 1 1 0</p> <p>1 0 0 0 0</p> <p>1 0 0 1 1</p> <p>1 0 1 0 1</p> <p>1 0 1 1 0</p> <p>1 1 0 0 1</p> <p>1 1 0 1 0</p> <p>1 1 1 0 0</p> <p>1 1 1 1 1</p>	<p>EJERCICIO 2.1</p> <p>A B C D Y</p> <p>-----</p> <p>0 0 0 0 1</p> <p>0 0 0 1 0</p> <p>0 0 1 0 0</p> <p>0 0 1 1 0</p> <p>0 1 0 0 0</p> <p>0 1 0 1 0</p> <p>0 1 1 0 0</p> <p>0 1 1 1 0</p> <p>1 0 0 0 1</p> <p>1 0 0 1 1</p> <p>1 0 1 0 1</p> <p>1 0 1 1 1</p> <p>1 1 0 0 1</p> <p>1 1 0 1 1</p> <p>1 1 1 0 1</p> <p>1 1 1 1 0</p>	<p>EJERCICIO 2.3</p> <p>A B C D Y</p> <p>-----</p> <p>0 0 0 0 0</p> <p>0 0 0 1 1</p> <p>0 0 1 0 0</p> <p>0 0 1 1 0</p> <p>0 1 0 0 1</p> <p>0 1 0 1 1</p> <p>0 1 1 0 1</p> <p>0 1 1 1 1</p> <p>1 0 0 0 0</p> <p>1 0 0 1 1</p> <p>1 0 1 0 0</p> <p>1 0 1 1 1</p> <p>1 1 0 0 1</p> <p>1 1 0 1 1</p> <p>1 1 1 0 1</p> <p>1 1 1 1 1</p>
<p>EJERCICIO 1.2</p> <p>A B C Y</p> <p>-----</p> <p>0 0 0 1</p> <p>0 0 1 1</p> <p>0 1 0 0</p> <p>0 1 1 0</p> <p>1 0 0 1</p> <p>1 0 1 1</p> <p>1 1 0 0</p> <p>1 1 1 0</p>	<p>EJERCICIO 1.4</p> <p>A B C D Y</p> <p>-----</p> <p>0 0 0 0 0</p> <p>0 0 0 1 0</p> <p>0 0 1 0 0</p> <p>0 0 1 1 0</p> <p>0 1 0 0 0</p> <p>0 1 0 1 0</p> <p>0 1 1 0 0</p> <p>0 1 1 1 0</p> <p>1 0 0 0 1</p> <p>1 0 0 1 0</p> <p>1 0 1 0 0</p> <p>1 0 1 1 0</p> <p>1 1 0 0 1</p> <p>1 1 0 1 1</p> <p>1 1 1 0 1</p>	<p>EJERCICIO 2.2</p> <p>A B C Y</p> <p>-----</p> <p>0 0 0 1</p> <p>0 0 1 1</p> <p>0 1 0 0</p> <p>0 1 1 1</p> <p>1 0 0 1</p> <p>1 0 1 1</p> <p>1 1 0 0</p> <p>1 1 1 1</p>	<p>EJERCICIO 2.4</p> <p>A B C Y</p> <p>-----</p> <p>0 0 0 1</p> <p>0 0 1 0</p> <p>0 1 0 1</p> <p>0 1 1 1</p> <p>1 0 0 0</p> <p>1 0 1 0</p> <p>1 1 0 1</p> <p>1 1 1 1</p>

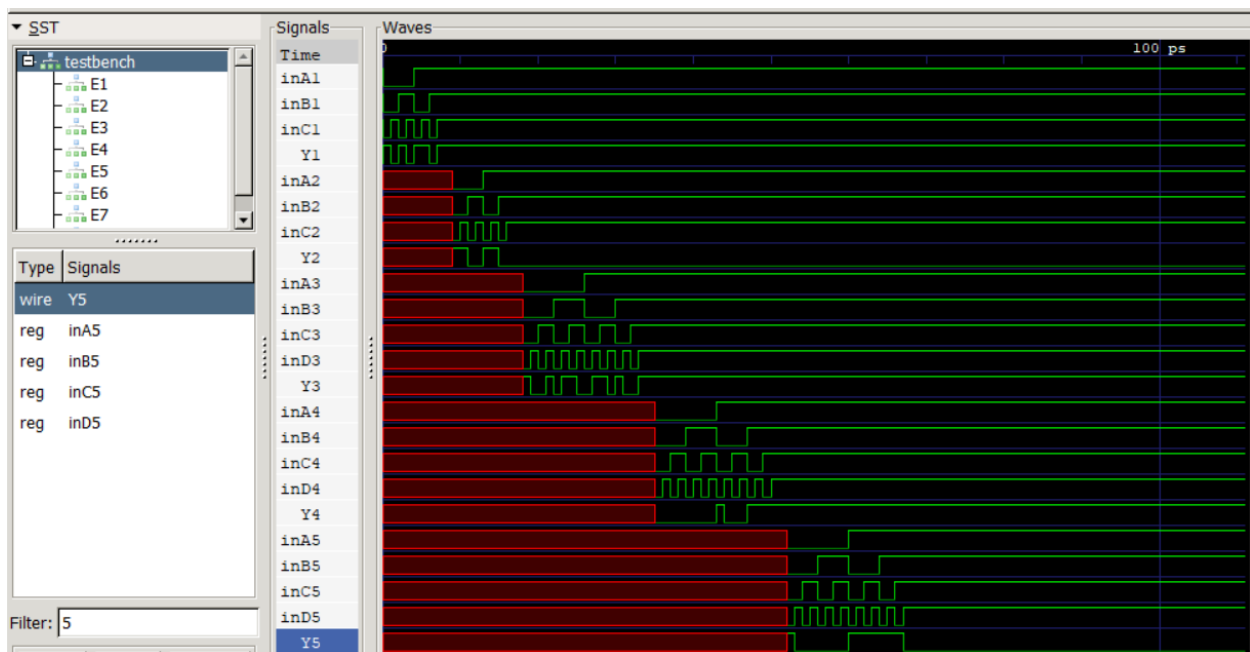

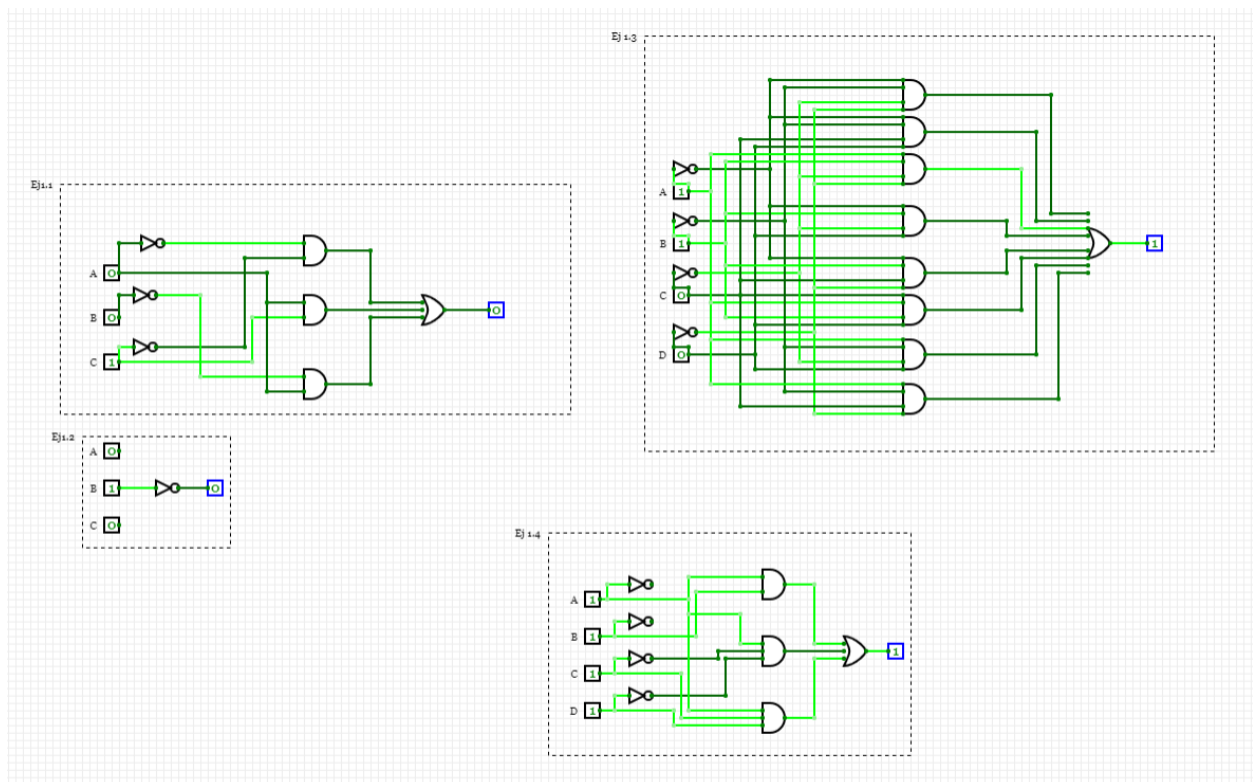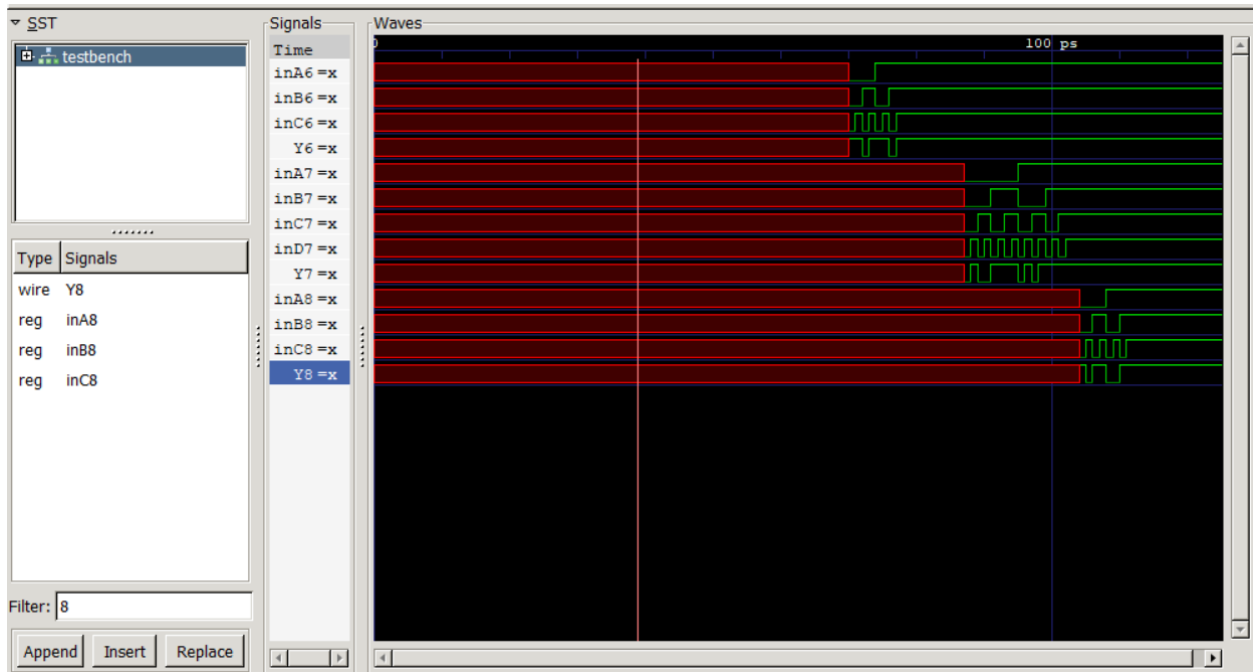

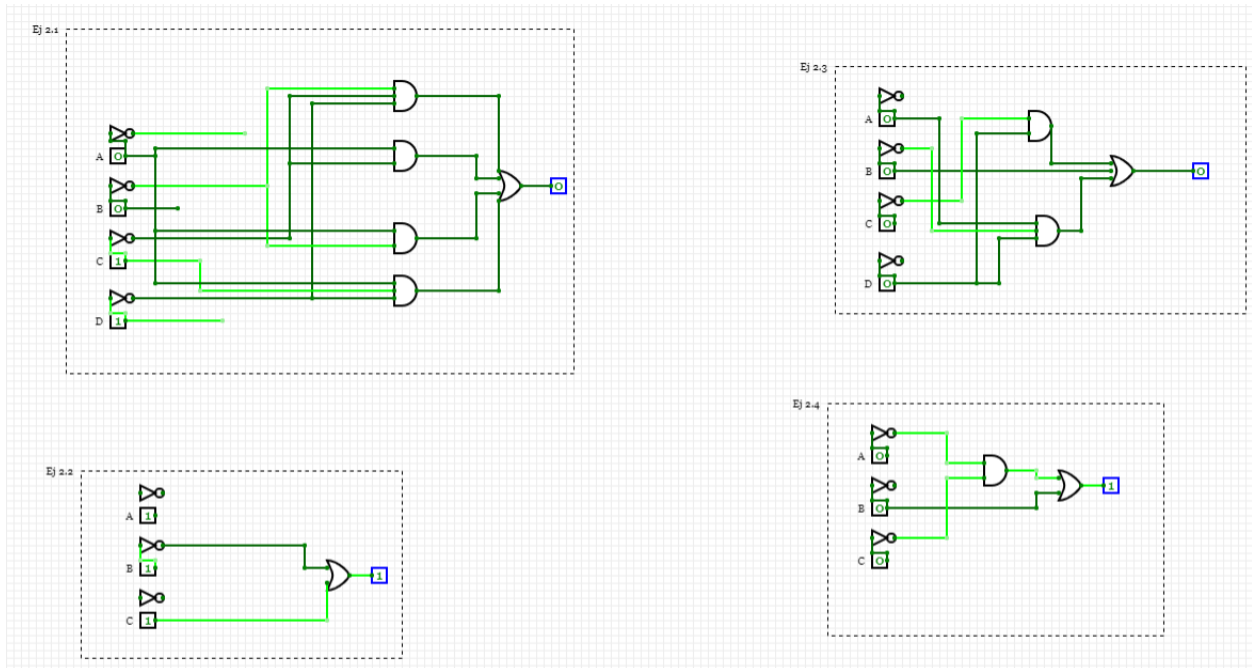

Ejercicio 5

A	B	C	Y
Armado	Ventana	Movimiento	Alarma y Luces
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1

POS

$(A+B+C)(A+B+C')(A+B'+C)(A+B'+C')(A'+B'+C)$

SOP

$(AB'C')+(AB'C)+(ABC)$

A	B	C	Y
Armado	Ventana	Movimiento	Alarma y Luces
0	x	x	0
1	0	x	1
1	1	0	0
1	1	1	1

C

		AB			
		00	01	11	10
0		0	0	0	1
1		0	0	1	1

Y=AC+AB'

```

//Diego Alejandro Mendez
//Carnet 19673
//Ejercicio 05

module MK_GL(input wire A,B,C, output wire Y);
//Mapa Karnaugh con Gate Modeling

    wire out01, out02, out03, out04, out05, AN, BN, CN;

//Not's
    not U1(AN,A);
    not U2(BN,B);
    not U3(CN,C);

//Compuerta
    and U4(out01,A,C);
    and U5(out02,A,BN);
    or U6(Y, out01, out02);

endmodule //MK_GL

module MK_OP(input wire A,B,C, output wire Y);
//Mapa de Karnaugh con Operadores

    assign Y= (A & C) | (A & ~B);

endmodule //MK_OP

module SOP_GL(input wire A,B,C, output wire Y);
//SOP con Gate Modeling

wire out01, out02, out03, out04, out05, AN, BN, CN;

//Not's
    not U1(AN,A);
    not U2(BN,B);
    not U3(CN,C);

//Compuerta
    and U4(out01,A,BN,CN);
    and U5(out02,A,BN,C);
    and U6(out03,A,B,C);
    or U6(Y, out01, out02, out03);

endmodule // SOP_GL

```

```

module SOP_OP (input wire A,B,C, output wire Y);
//SOP con Operadores

    assign Y = (A & ~B & ~C) | (A & ~B & C) | (A & B & C);

endmodule // SOP_OP

module POS_GL (input wire A,B,C, output wire Y);
//POS con Gate
    wire out01, out02, out03, out04, out05, AN, BN, CN;

//Not's
    not U1(AN,A);
    not U2(BN,B);
    not U3(CN,C);

//Compuerta
    or U4(out01,A,B,C);
    or U5(out02,A,B,CN);
    or U6(out03,A,BN,C);
    or U6(out04,A,BN,CN);
    or U7(out05,AN,BN,C);
    and U8(Y,out01, out02, out03, out04, out05);

endmodule //POS_GL

module POS_OP (input wire A,B,C, output wire Y);
//POS con Operadores

    assign Y = (A | B | C) & (A | B | ~C) & (A | ~B | C) & (A | ~B | ~C) & (~A | ~B | C);

endmodule //POS_OP

```

```

//Diego Alejandro Mendez
//Carnet 19673
//Ejercicio 05

module testbench();
// registrar entradas
    reg inA1, inB1, inC1;
    reg inA2, inB2, inC2;
    reg inA3, inB3, inC3;
    reg inA4, inB4, inC4;
    reg inA5, inB5, inC5;
    reg inA6, inB6, inC6;

    wire Y1, Y2, Y3, Y4, Y5, Y6;

    MK_GL U1(inA1, inB1, inC1, Y1);
    MK_OP U2(inA2, inB2, inC2, Y2);
    SOP_GL U3(inA3, inB3, inC3, Y3);
    SOP_OP U4(inA4, inB4, inC4, Y4);
    POS_GL U5(inA5, inB5, inC5, Y5);
    POS_OP U6(inA6, inB6, inC6, Y6);

    initial begin //iniciamos el módulo MK_GL
        $display(" ");
        $display("Mapa Karnaugh de Gate Modeling");
        $display("A B C | Y");
        $display("-----");
        $monitor("%b %b %b %b",inA1,inB1,inC1,Y1);
        inA1=0; inB1=0; inC1=0;
        #1 inA1=0; inB1=0; inC1=1;
        #1 inA1=0; inB1=1; inC1=0;
        #1 inA1=0; inB1=1; inC1=1;
        #1 inA1=1; inB1=0; inC1=0;
        #1 inA1=1; inB1=0; inC1=1;
        #1 inA1=1; inB1=1; inC1=0;
        #1 inA1=1; inB1=1; inC1=1;
    end

```

```

initial begin    //iniciamos el módulo MK_OP
    #9
    $display("");
    $display("Mapa Karnaugh de Operadores");
    $display("A B C | Y");
    $display("-----");
    $monitor("%b %b %b  %b",inA2,inB2,inC2,Y2);
        inA2=0; inB2=0; inC2=0;
    #1 inA2=0; inB2=0; inC2=1;
    #1 inA2=0; inB2=1; inC2=0;
    #1 inA2=0; inB2=1; inC2=1;
    #1 inA2=1; inB2=0; inC2=0;
    #1 inA2=1; inB2=0; inC2=1;
    #1 inA2=1; inB2=1; inC2=0;
    #1 inA2=1; inB2=1; inC2=1;
end

initial begin
    #18
    $display(" ");          //iniciamos el módulo SOP_GL
    $display("SOP con Gate Modeling");
    $display("A B C | Y");
    $display("-----");
    $monitor("%b %b %b  %b",inA3,inB3,inC3,Y3);
        inA3=0; inB3=0; inC3=0;
    #1 inA3=0; inB3=0; inC3=1;
    #1 inA3=0; inB3=1; inC3=0;
    #1 inA3=0; inB3=1; inC3=1;
    #1 inA3=1; inB3=0; inC3=0;
    #1 inA3=1; inB3=0; inC3=1;
    #1 inA3=1; inB3=1; inC3=0;
    #1 inA3=1; inB3=1; inC3=1;
end

```

```

initial begin                                //iniciamos el SOP con Operadores
#27
    $display(" ");
    $display("SOP con Operadores");
    $display("A B C | Y");
    $display("-----");
    $monitor("%b %b %b %b",inA4,inB4,inC4,Y4);
    inA4=0; inB4=0; inC4=0;
    #1 inA4=0; inB4=0; inC4=1;
    #1 inA4=0; inB4=1; inC4=0;
    #1 inA4=0; inB4=1; inC4=1;
    #1 inA4=1; inB4=0; inC4=0;
    #1 inA4=1; inB4=0; inC4=1;
    #1 inA4=1; inB4=1; inC4=0;
    #1 inA4=1; inB4=1; inC4=1;
end

initial begin                                //iniciamos el POS con Gate Modeling
#36
    $display(" ");
    $display("POS con Gate Modeling");
    $display("A B C | Y");
    $display("-----");
    $monitor("%b %b %b %b",inA5,inB5,inC5,Y5);
    inA5=0; inB5=0; inC5=0;
    #1 inA5=0; inB5=0; inC5=1;
    #1 inA5=0; inB5=1; inC5=0;
    #1 inA5=0; inB5=1; inC5=1;
    #1 inA5=1; inB5=0; inC5=0;
    #1 inA5=1; inB5=0; inC5=1;
    #1 inA5=1; inB5=1; inC5=0;
    #1 inA5=1; inB5=1; inC5=1;
end

```

```

initial begin
    #45
    $display(" ");          //iniciamos el módulo POS con Operadores
    $display("POS con Operadores");
    $display("A B C | Y");
    $display("-----");
    $monitor("%b %b %b   %b",inA6,inB6,inC6,Y6);
    inA6=0; inB6=0; inC6=0;
    #1 inA6=0; inB6=0; inC6=1;
    #1 inA6=0; inB6=1; inC6=0;
    #1 inA6=0; inB6=1; inC6=1;
    #1 inA6=1; inB6=0; inC6=0;
    #1 inA6=1; inB6=0; inC6=1;
    #1 inA6=1; inB6=1; inC6=0;
    #1 inA6=1; inB6=1; inC6=1;
end

initial
#54 $finish;


initial begin

    $dumpfile("Ejercicio_tb.vcd");
    $dumpvars(0,testbench);
end


endmodule

```



	SOP con Gate Modeling	POS con Gate Modeling
Mapa Karnaugh de Gate Modeling	A B C Y	A B C Y
A B C Y	-----	-----
-----	0 0 0 0	0 0 0 0
VCD info: dumpfile Ejercicio_tb.	0 0 1 0	0 0 1 0
0 0 0 0	0 1 0 0	0 1 0 0
0 0 1 0	0 1 1 0	0 1 1 0
0 1 0 0	1 0 0 1	1 0 0 1
0 1 1 0	1 0 1 1	1 0 1 1
1 0 0 1	1 1 0 0	1 1 0 0
1 0 1 1	1 1 1 1	1 1 1 1
1 1 0 0		
1 1 1 1		
	SOP con Operadores	POS con Operadores
Mapa Karnaugh de Operadores	A B C Y	A B C Y
A B C Y	-----	-----
-----	0 0 0 0	0 0 0 0
0 0 0 0	0 0 1 0	0 0 1 0
0 0 1 0	0 1 0 0	0 1 0 0
0 1 0 0	0 1 1 0	0 1 1 0
0 1 1 0	1 0 0 1	1 0 0 1
1 0 0 1	1 0 1 1	1 0 1 1
1 0 1 1	1 1 0 0	1 1 0 0
1 1 0 0	1 1 1 1	1 1 1 1
1 1 1 1		

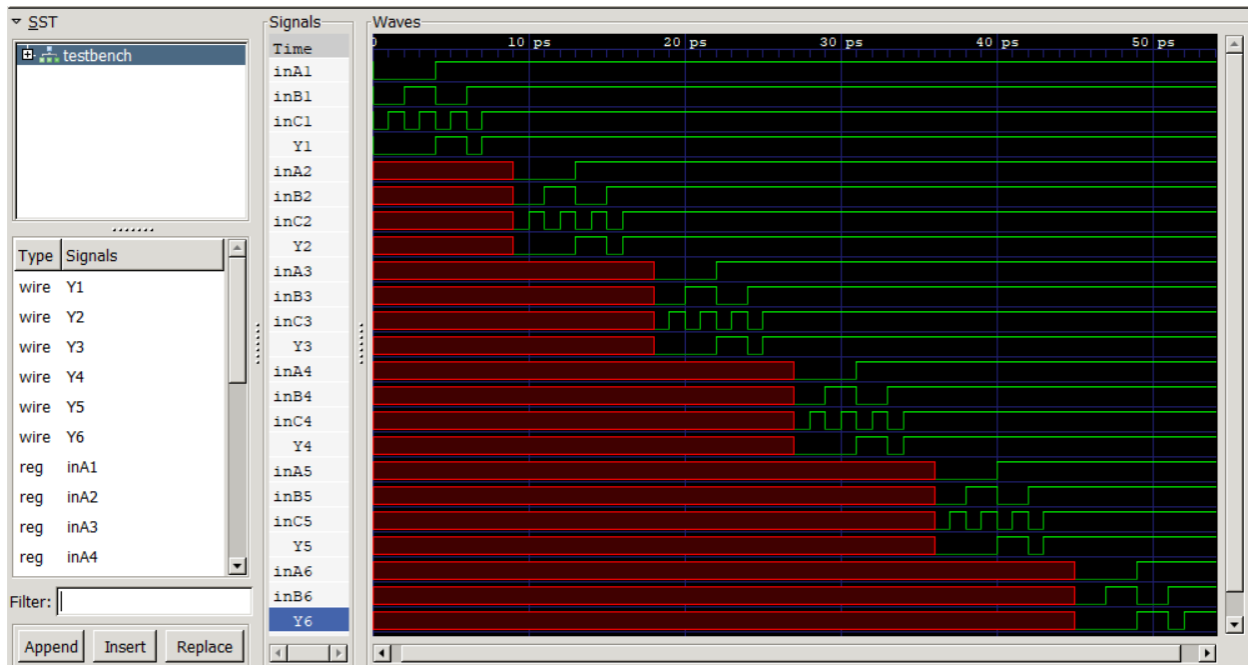

POS

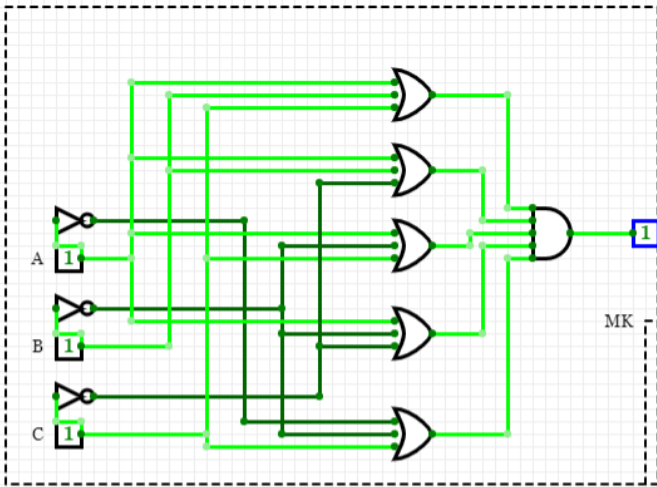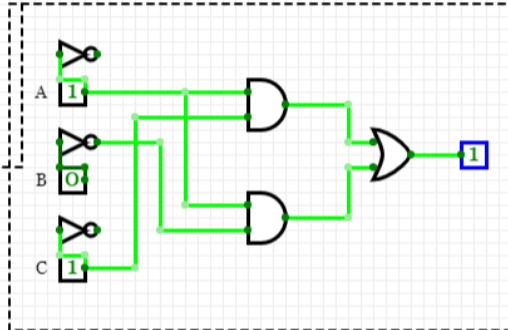

MK



SOP

